

REACTIVE PARTS AND FILTERING

How capacitors and inductors react to changing signals, and how an RC filter's cutoff frequency picks what passes. With a live calculator.

ONE THOUSAND DRONES ENGINEERING TEAM · VERIFIED 2026-07

Resistors treat every frequency the same. Capacitors and inductors do not: they react to how fast a signal changes, and that lets you build a filter that passes some frequencies and blocks others.

REACTANCE

A capacitor's opposition to current falls as the frequency rises, and an inductor's opposition rises. That frequency-dependent opposition is reactance. It is why a capacitor blocks steady DC but passes a fast signal.

THE RC FILTER AND ITS CUTOFF

A resistor and a capacitor together set a cutoff frequency, the point where the filter starts to roll off. In a low-pass filter, frequencies below the cutoff pass and frequencies above it are attenuated. The cutoff comes straight from the R and C values.

$$f_c = 1 / (2 \times \pi \times R \times C)$$

CALCULATOR · RC FILTER CUTOFF FREQUENCY CALCULATOR (FIRST-ORDER)

Find a first-order RC filter's -3 dB cutoff ($f_c = 1 / 2\pi RC$) and time constant from R and C. For ADC anti-alias and noise filtering.

Interactive calculator: academy.onethousanddrones.com/tools/rc-filter-cutoff

FIND AN RC FILTER'S CUTOFF FREQUENCY AND TIME CONSTANT.

A mechanical picture makes the roll-off intuitive: an RC low-pass behaves like a shock absorber. A fast, sharp jolt gets soaked up and smoothed, while a slow, steady change passes straight through unaltered. Fast is above the cutoff and gets damped; slow is below it and gets through.

WHERE YOU MEET IT

An RC low-pass in front of an ADC is an anti-alias filter: it removes fast noise the converter would otherwise fold into the signal (Espressif ESP-IDF). The same RC also sets how fast a line settles, which is why a reset or button line often carries one.

- [Espressif. ESP-IDF Programming Guide: ESP32-S3 Analog to Digital Converter \(ADC\).](https://docs.espressif.com) docs.espressif.com

► FUNDAMENTALS · REACTANCE & FILTERS

REACTIVE PARTS AND FILTERING

LOW FREQ · PASSES



HIGH FREQ · BLOCKED



A cap reacts to how fast a signal changes. An RC filter passes slow signals and shrinks fast ones; the corner is $f_c = 1 / (2\pi R C)$.

AN RC LOW-PASS PASSES LOW FREQUENCIES AND ROLLS OFF ABOVE THE CUTOFF.

CHECKPOINT

1. Reactance is what?

- a. A resistor's fixed opposition to current
- b. A frequency-dependent opposition to current**
- c. The heat a part gives off

ANSWER · B

A capacitor's and inductor's opposition changes with frequency; that is reactance.

2. In a low-pass RC filter, which frequencies pass?

- a. Those above the cutoff
- b. All frequencies equally
- c. Those below the cutoff**

ANSWER · C

Low-pass passes below the cutoff and attenuates above it.

3. An RC filter in front of an ADC does what?

- a. Removes fast noise before the converter samples it
- b. Amplifies the signal
- c. Stores the reading

ANSWER · A

It is an anti-alias filter: it strips high-frequency noise the ADC would otherwise fold in.

- Prerequisite: capacitors and decoupling
- Calculate it: the RC filter cutoff calculator
- Next: grounds and power rails